 



VE270 Lecture 8 Counter

Asynchronous Binary Counter


T-Flip-Flops implementation



D-Flip-Flops implementation

 

Problem: Delays

 

Synchronous Binary Counter

Design (With D-Flip-Flop)

Present State			Next State			D flip flop input		
Q2	Q1	Q0	Q2 ⁺	Q1 ⁺	Q0 ⁺	D2	D1	D0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

With the Present State as the D flip flop output.


Apply K-Map method:

Q1Q0	00	01	11	10
Q2=0	0	0	1	0
Q2=1	1	1	0	1


Q1Q0	00	01	11	10
Q2=0	0	1	0	1
Q2=1	1	0	0	1

Q1Q0	00	01	11	10
Q2=0	1	0	0	1
Q2=1	1	0	0	1

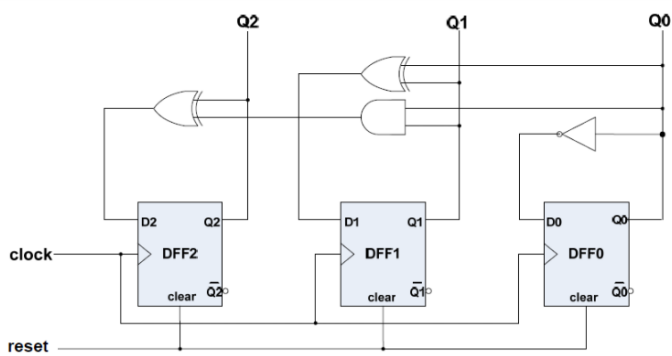
So we get $D_n = Q_n \oplus (Q_{n-1} \cdots Q_n)$



External Control

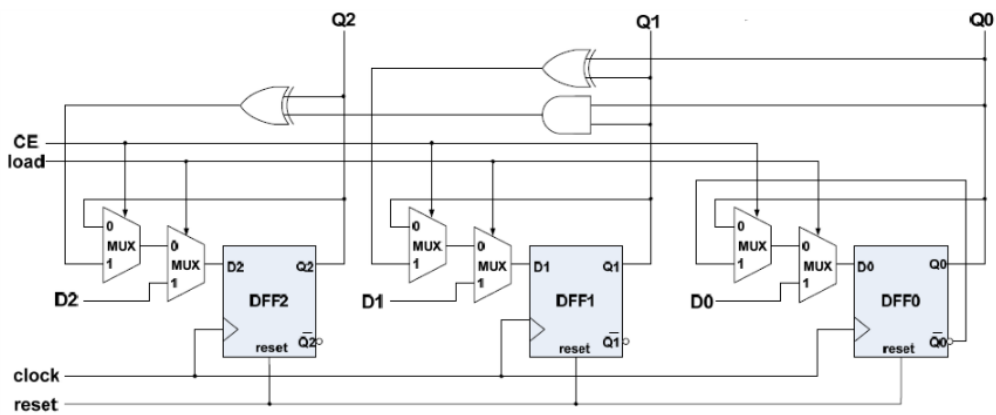



Customize Counting Sequence

 


Q2	Q1	Q0	Q2 ⁺	Q1 ⁺	Q0 ⁺
0	0	0	X	X	X
0	0	1			
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	0	1	0
1	1	0	X	X	X
1	1	1			

Clock Divider

  Divide by n , let the load is activated by $n - 1$.




Output Synchronization

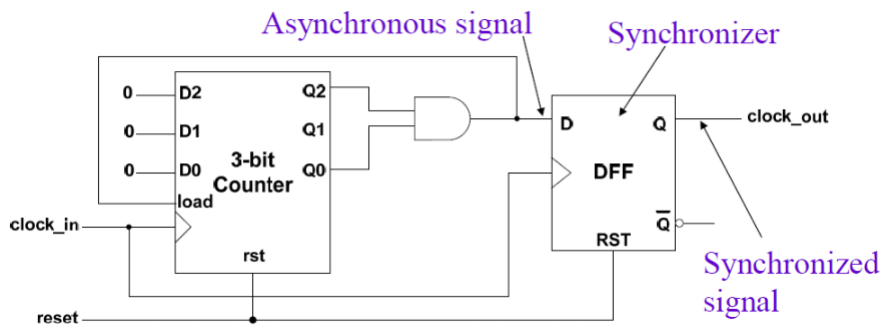

Since the output clock signal may have delay by the gate, so we give a D-Flip-Flop to synchronize the signal to the output.

The output still have delay, but the delay is smaller, not deleted.

Up/Down Counter

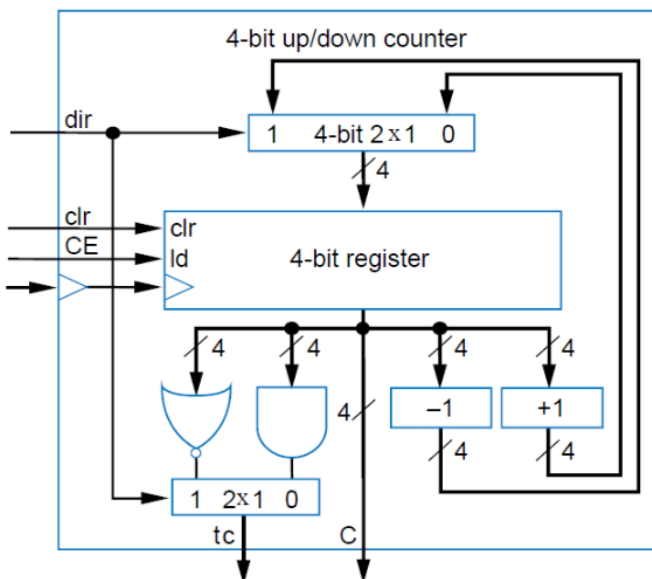

Alternative Design Counter with Control

