 



# VE270 Lecture 6 Latches and Flip Flops

## Reality of Combinational Circuit: Non-Ideal Gate Behavior: Delay



## Bit Storage


### An Unsuccessful Attempt

 



So due to the feedback on combinational circuit, the output (real, not ideal) is decided by

- Present Inputs
- Past Input Sequence
- Past Output Sequence
 
## SR Latch: Second Attempt at Bit Storage



Then we can implement a circuit:

  

But what will happen if  $S=1$  and  $R=1$  simultaneously.

## Representation of SR Latch

When discussing about latches and flip-flops, we use



- **present state** to represent **current value of Q output**
- **next state** to represent **new value of Q output** responding to **current inputs** and **feedback of current output**

S(t)	R(t)	Q(t)	Q(t+Δ)	→ Q <sup>+</sup>
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	X	not allowed
1	1	1	X	

		S(t)	
		0	1
R(t) Q(t)	00	0	1
	01	1	1
	11	0	X
	10	0	X


So  $Q^+ = S + R'Q$ .
  
## Alternative Implementation of SR Latch




S	R	Q	Q <sup>+</sup>	
0	0	0	X	not allowed
0	0	1	X	
0	1	0	1	set
0	1	1	1	
1	0	0	0	reset
1	0	1	0	
1	1	0	0	hold
1	1	1	1	

## Gated SR Latch

 

Characteristic Table


G	S	R	Q <sup>+</sup>
0	x	x	Q; Latch locked
1	0	0	Q; Hold state
1	0	1	0; Reset state
1	1	0	1; Set state
1	1	1	not allowed

 

Gated SR latch symbol

 
## Solution for SR Latch Restriction: Gated D Latch

A solution to the unstable state problem caused by  $S = R = 1$  in  $SR$  Latch



Characteristic Table		
G	D	Q <sup>+</sup>
1	0	0
1	1	1
0	X	Q

 - The input value is stored into the latch only when gate control G has high level – **Level Sensitive**




D latch symbol

 
## Gated D Latch - Transparent Latch

properties:


- temporary storage of a bit
- The binary information at the data input of the D latch is **copied to** the Q output when the control input G is high (or enabled)
- The output Q follows changes on the data input D as long as the control input G is enabled, so called a **transparent latch**.



## Control Input - Clock Signal

 


## Problem with Level-Sensitive D Latch

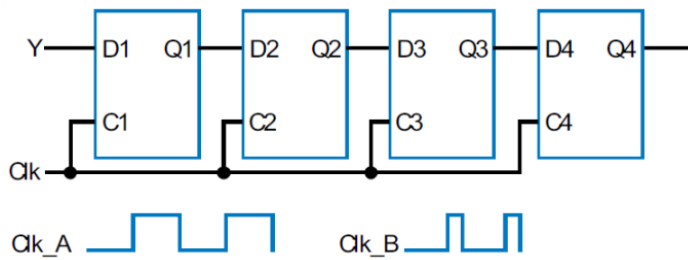

So if the time length of Clk is short, the signal will go through fewer latches.

It is hard to control storage elements.

## Rising-Edge Triggered D Flip Flop

 


with the characteristic equation:  $Q^+ = D$  at active clock edges

clock	D	$Q^+$
$\uparrow$	0	0
$\uparrow$	1	1
0	X	Q
1	X	Q


## Properties of Rising-Edge triggered D Flip Flop

- The output changes only at the **rising edges of the clock signal**.
- The output Q gives the value of input D at the time point of rising edge of clock.

## D Flip-Flop Symbols

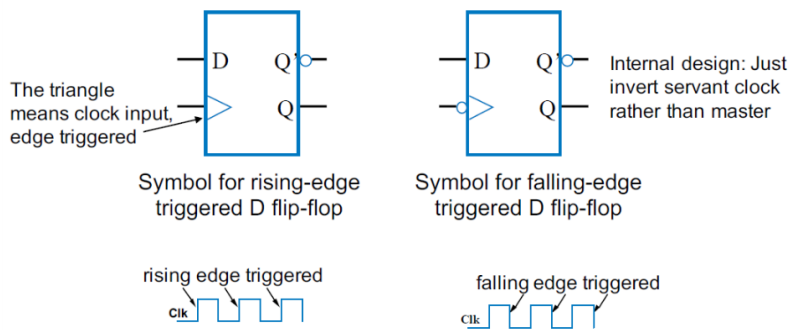


## Application of D Flip-Flop

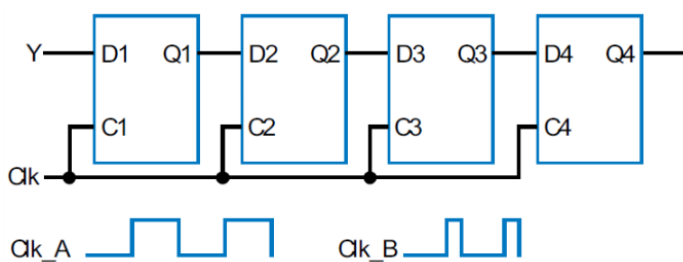


Check back to D Latch problem, then it ignore the  $Clk = 1$  time length, just focus on rising edge.
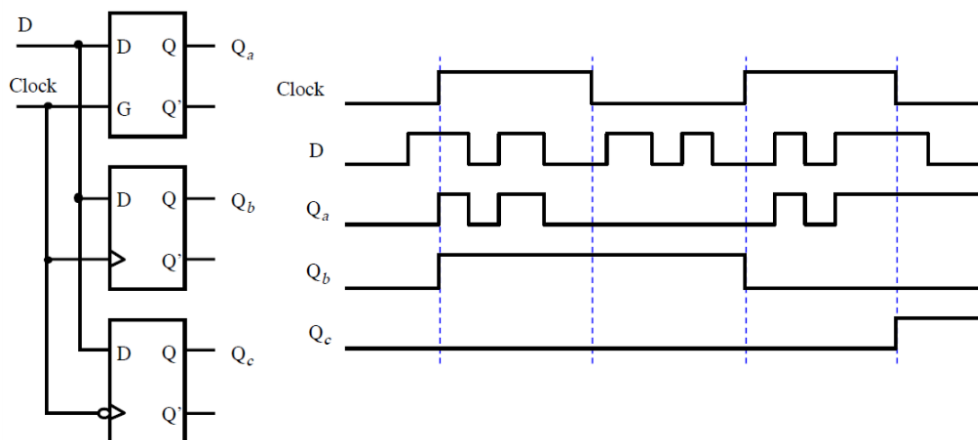
## Flip Flop & Latch

- Flip Flop
  - **edge-sensitive**, input only focus on active edges (rising/falling)
  - behaviors are **synchronous** to the clock signal (synchronous is because it has clock signal)
- Latch
  - **level-sensitive**, input matters whenever control has active level (high/low)
  - behaviors are **asynchronous** to the clock signal (asynchronous is because it doesn't have clock signal)




 
## A D Flip-Flop Implemented Flight-Attendant Call Button



Call	Cancel	Q	$Q^+ = D$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


## Rising Edge-triggered JK Flip Flop

  


J	K	$Q^+$
0	0	Q
0	1	0
1	0	1
1	1	$Q'$

Characteristic equation:  
 $Q^+ = JQ' + K'Q$


## Rising Edge-triggered T Flip Flop

 

Implemented with D ff

 


Implemented with JK ff

 


clock	T	$Q^+$
$\uparrow$	0	Q
$\uparrow$	1	$Q'$

 Characteristic equation:  
 $Q^+ = T'Q + TQ' = T \oplus Q$



 
## Basic Register

Multiple Flip-Flops sharing same clock signal.




Then we can set register:

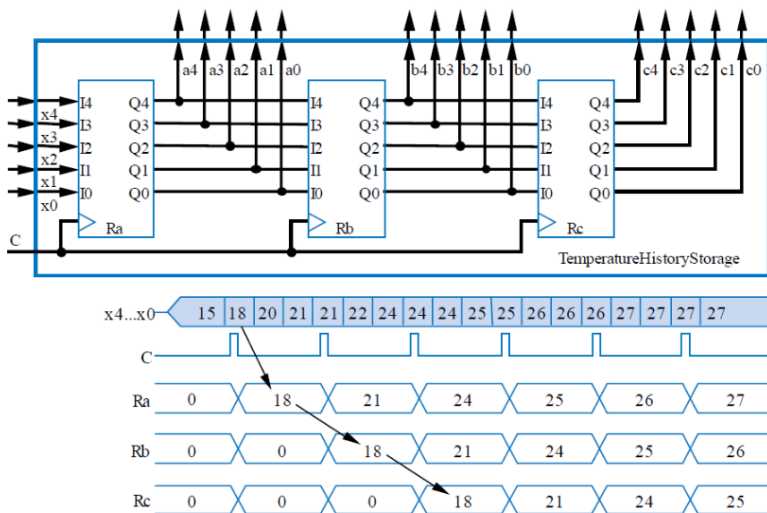
 
## Control Input for Flip Flops


- Asynchronous: control signals do not depend on clock signal
- Synchronous: control signals depend on the clock signal
- Active low: it controls when it is low
- Active high: it controls when it is high





 
## Asynchronous Control Implement

Control signals decides the output value directly independent of the clock signal




 D Flip Flop with active low asynchronous Clear


 
## Synchronous Control Implement

Synchronous clear: control signal depends on the active edge (either rising or falling) of the clock signal.



D Flip Flop with active low synchronous Clear.

