 


VE270 Lecture 11 FSM Optimizations


Optimization by State Reduction



Moore and Mealy FSMs

Check FSM circuit:

 
- **Next state logic** is defined by the **current state logic** and **FSM inputs**.
- Output logic:
 - **Moore logic FSM**: it depends on **present state** only.
 - **Mealy logic FSM**: it depends on **present state** and **FSM inputs**.



Moore FSM		Mealy FSM																																																																									
<p>State Diagram</p> <p>State Table</p> <table> <tr> <th>In</th><th>P.S.</th><th>N.S.</th><th>Out</th></tr> <tr><td>0</td><td>S0</td><td>S3</td><td>0</td></tr> <tr><td>1</td><td>S0</td><td>S1</td><td>0</td></tr> <tr><td>0</td><td>S1</td><td>S0</td><td>1</td></tr> <tr><td>1</td><td>S1</td><td>S2</td><td>0</td></tr> <tr><td>0</td><td>S2</td><td>S1</td><td>0</td></tr> <tr><td>1</td><td>S2</td><td>S2</td><td>0</td></tr> <tr><td>0</td><td>S3</td><td>S2</td><td>0</td></tr> <tr><td>1</td><td>S3</td><td>S1</td><td>1</td></tr> </table>		In	P.S.	N.S.	Out	0	S0	S3	0	1	S0	S1	0	0	S1	S0	1	1	S1	S2	0	0	S2	S1	0	1	S2	S2	0	0	S3	S2	0	1	S3	S1	1	<p>State Diagram</p> <p>State Table</p> <table> <tr> <th>In</th><th>P.S.</th><th>N.S.</th><th>Out</th></tr> <tr><td>0</td><td>S0</td><td>S0</td><td>0</td></tr> <tr><td>1</td><td>S0</td><td>S1</td><td>1</td></tr> <tr><td>0</td><td>S1</td><td>S1</td><td>1</td></tr> <tr><td>1</td><td>S1</td><td>S2</td><td>0</td></tr> <tr><td>0</td><td>S2</td><td>S0</td><td>1</td></tr> <tr><td>1</td><td>S2</td><td>S3</td><td>0</td></tr> <tr><td>0</td><td>S3</td><td>S3</td><td>0</td></tr> <tr><td>1</td><td>S3</td><td>S1</td><td>1</td></tr> </table>		In	P.S.	N.S.	Out	0	S0	S0	0	1	S0	S1	1	0	S1	S1	1	1	S1	S2	0	0	S2	S0	1	1	S2	S3	0	0	S3	S3	0	1	S3	S1	1
In	P.S.	N.S.	Out																																																																								
0	S0	S3	0																																																																								
1	S0	S1	0																																																																								
0	S1	S0	1																																																																								
1	S1	S2	0																																																																								
0	S2	S1	0																																																																								
1	S2	S2	0																																																																								
0	S3	S2	0																																																																								
1	S3	S1	1																																																																								
In	P.S.	N.S.	Out																																																																								
0	S0	S0	0																																																																								
1	S0	S1	1																																																																								
0	S1	S1	1																																																																								
1	S1	S2	0																																																																								
0	S2	S0	1																																																																								
1	S2	S3	0																																																																								
0	S3	S3	0																																																																								
1	S3	S1	1																																																																								

Problem Example

 - Example: design a non-overlapping sequence detector as Mealy FSM




- Z is determined every three bits, $Z = 1$, as soon as an input sequence 101 is detected

X =	0	0	1	1	0	1	0	0	1	0	1	0	0	1	0
Z =	0	0	0	0	0	1	0	0	0	0	1	0	0	0	0
time	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14

one input: X

one output: Z

Mealy FSM Design

 

it is the initial diagram, and we can use a state reduction table.


Two states are equivalent iff both next states and outputs are identical

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
A0	A4	A1	0	0
A1	A2	A5	0	0
A2	A0	A0	0	1
A3	A4	A1	0	0
A4	A5	A5	0	0
A5	A0	A0	0	0
A6	A4	A1	0	0

A0 → S0
A1 → S1
A2 → S2
A4 → S3
A5 → S4


Present State	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S3	S1	0	0
S1	S2	S4	0	0
S2	S0	S0	0	1
S3	S4	S4	0	0
S4	S0	S0	0	0

and we get new one:

 

After applying state register, we implement it into a circuit.

Moore FSM Design

 


successful path is the initial diagram

Present State	Next State		Output
	X=0	X=1	
A0	A4	A1	0
A1	A2	A5	0
A2	A0	A3	0
A3	A4	A1	1
A4	A5	A5	0
A5	A0	A0	0
A6	A4	A1	0

A0 → S0
A1 → S1
A2 → S2
A3 → S3
A4 → S4
A5 → S5

Present State	Next State		Output
	X=0	X=1	
S0	S4	S1	0
S1	S2	S5	0
S2	S0	S3	0
S3	S4	S1	1
S4	S5	S5	0
S5	S0	S0	0

reduces the states

 


successful path and here is the new diagram

Moore vs Mealy

- Output
 - Moore: Depends on current state
 - Mealy: Depends on current state and inputs
- State Diagram
 - Moore: More states → possibly bigger circuit
 - Mealy: Less states → possibly less number of flip-flops
- Speed of output response to the inputs
 - Moore: as long as one clock cycle delay
 - Mealy: quick, as soon as input changes
- Timing issue
 - Moore: synchronous, more stable
 - Mealy: asynchronous (also based on inputs), may cause serious problem

Combined Mealy and Moore

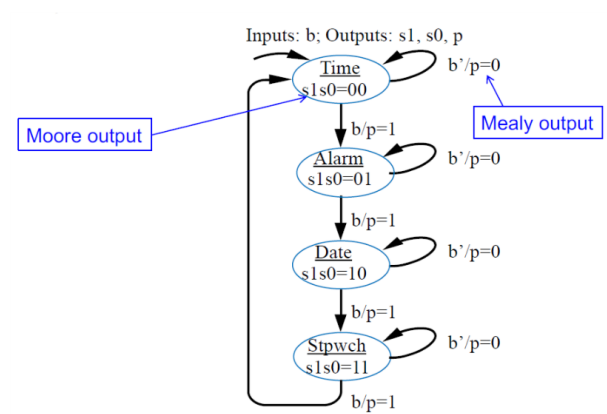


FSM Reverse Engineering

Given a circuit of FSM, we should find the behavior

- Mealy or Moore
- State number
- Logic for next state
- State table
- State diagram

Implication Table State Reduction

Inputs: x ; Outputs: y

 

Use implication tables to simplify the FSM.