

VE270 Lecture 12 Arithmetic Components

Carry Look-ahead Adder

Check the Carry-Ripple Adder, it is created with full adders.


For 4-bit adder, we add two 4-bit numbers and generate a 5-bit number (4-bit sum and 1-bit carry).

Faster Adder

Use two-level combinational logic design process.


- pro: fast
 - 2 gate level delays
- con: large
 - 9 inputs and 5 outputs.
 - Truth table would have $2^{4+4+1} = 512$ rows

Full Adder

 

sum is $\sum m(1, 2, 4, 7) = A \oplus B \oplus C$, carry is $\sum m(3, 5, 6, 7) = AB + AC + BC = (A \oplus B)C + AB$

 Faster Adder - Intuitive Attempt at "Look ahead"



Notice – no rippling of carry


Then we produce carries directly and recursively: $c_{n+1} = a_n b_n + a_n c_n + b_n c_n$

Two layer SOP logic.

Better Form of Look Ahead

Since we get the **Carry** $= ab + (a \oplus b)c$ then we define **Propagate** $P = a \oplus b$ and **Generate** $G = ab$.

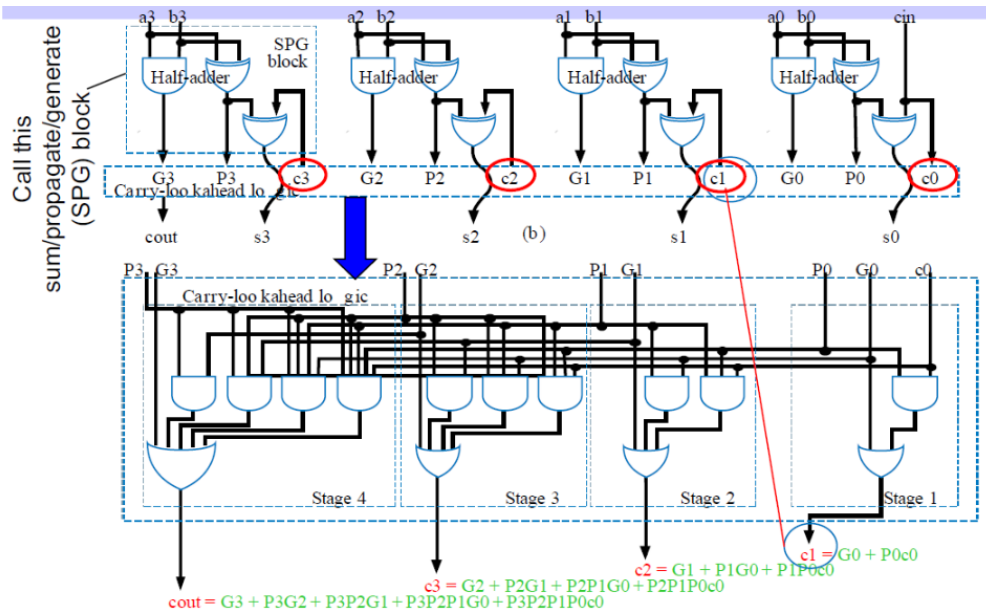
Then **Cout** $= G + Pc$, $c_{n+1} = G_n + P_n c_n$




So only 4 gate level delay, 2 from SPG block and 2 from look ahead block.

Cascading Adder

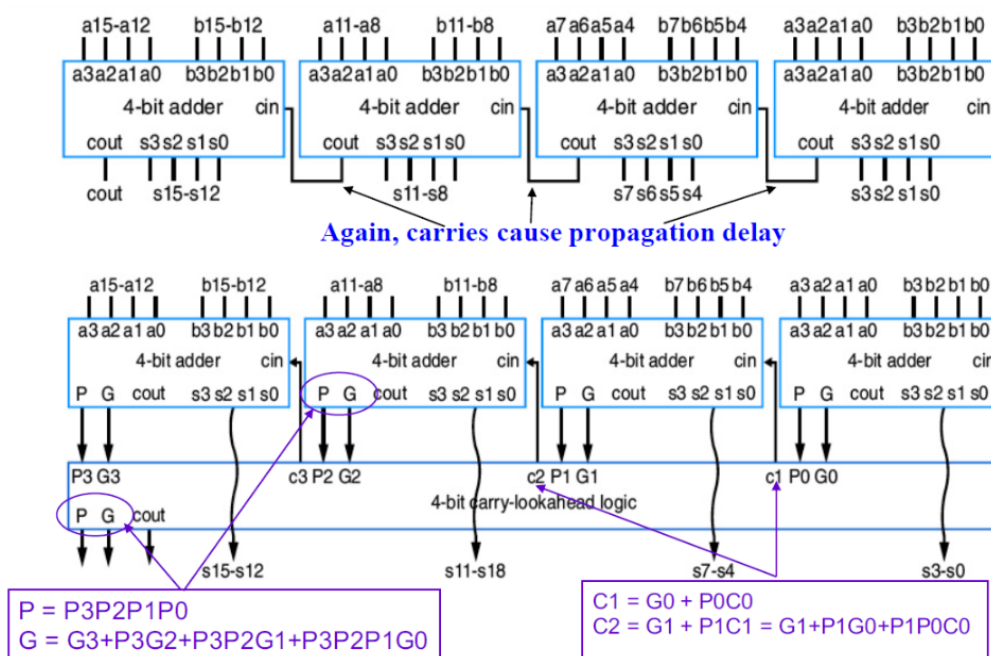
According to the $c = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$, we derive a P and G for cascading adder




CLA Multi-Level Adder

 

Incrementer

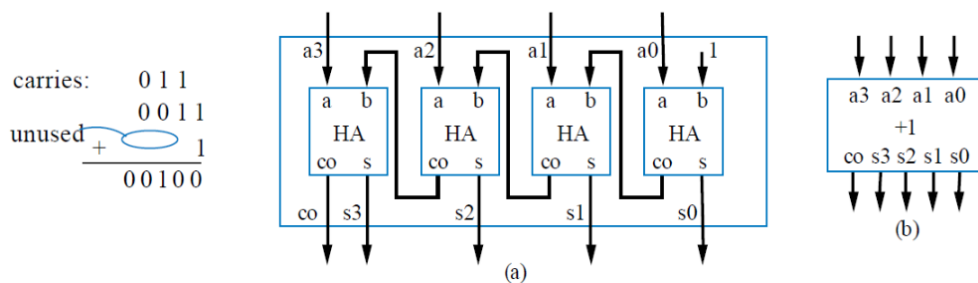


Multiplier - Array Style

 

Multiplier - Sequential (Add and Shift) Style

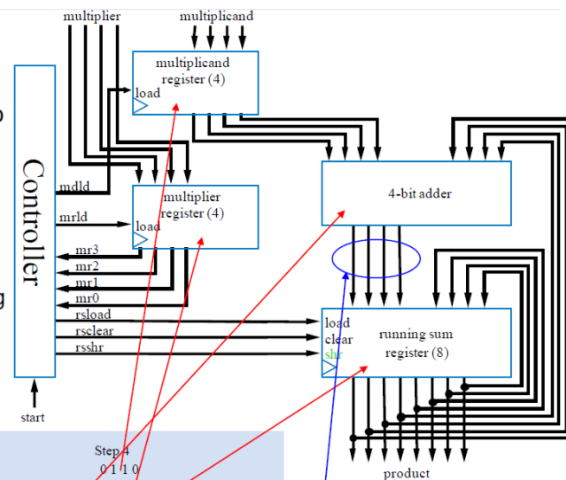
- Design circuit that computes one partial product at a time, adds to running sum
 - Note that **shifting** running sum right (relative to partial product) after each step ensures partial product added to correct running sum bits



Step 1	Step 2	Step 3	Step 4
0110	0110	0110	0110
+ 0011	+ 0011	+ 0011	+ 0011
0000	00110	010010	0010010
+ 0110	+ 0110	+ 0000	+ 0000
00110	010010	0010010	00010010
			(running sum)
			(partial product)
			(new running sum)

What about carry?

What if 2's complement?

 


ALU


Refer the Lecture 5, we can see an example for the ALU operations.

Problem, the mux will generate too much wires, wasting too much power.

Comparators

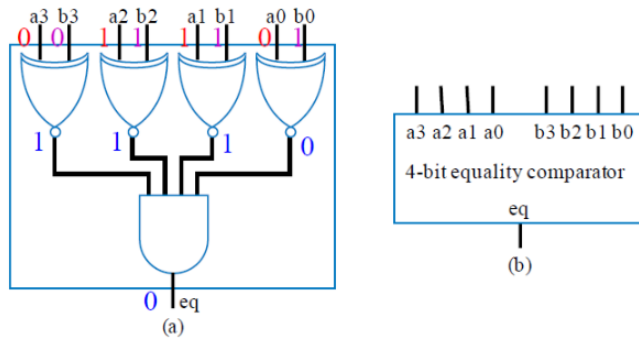

Magnitude Comparator

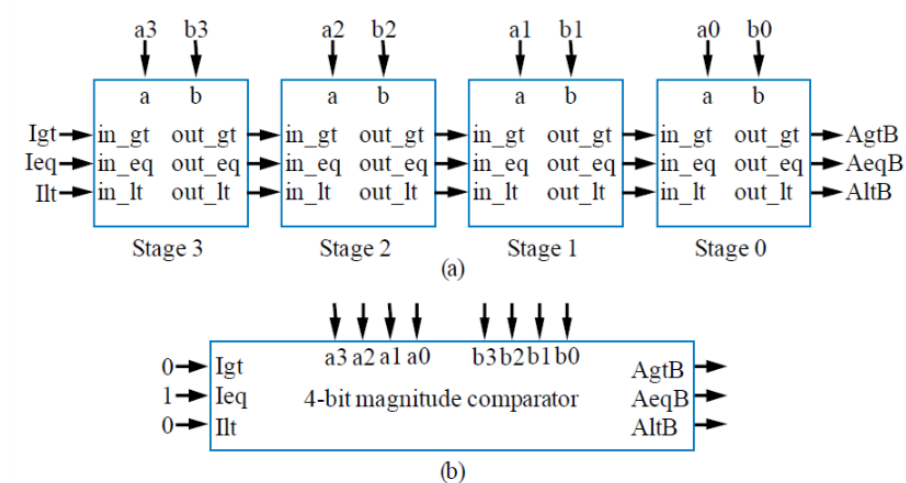

For each stage, we have:

- $out_gt = in_gt + (in_eq * a * b')$
- $out_eq = in_eq * (a \text{ XNOR } b)$
- $out_lt = in_lt + (in_eq * a' * b)$